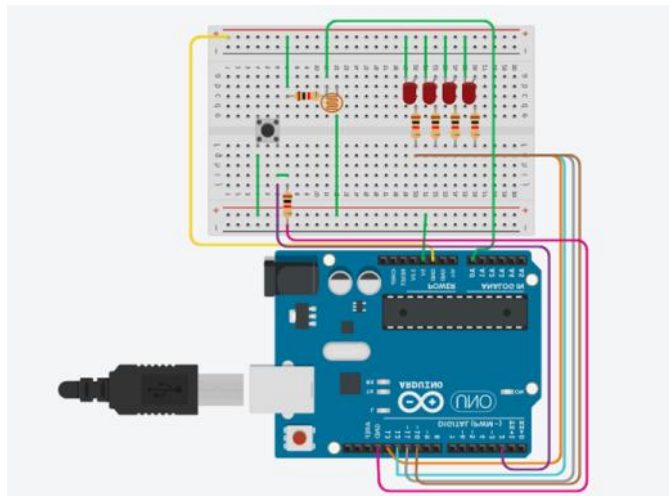


AIM:- Design an automatic night lighting system (with 4 connected leds) such the system is only activated when the master control switch is pressed. a) below 50% value of full brightness all leds constantly on. b) above 50% value of full brightness only first led is on.

Circuit Diagram:



Theory:

Concept Used:

- Ohm's law
- Kirchhoff's rule
- For loop

Learning & Observations:

- Working of Arduino
- Application of LDR

Problems & Troubleshooting:

- Port selection
- Loose connections
- Error in coding

Precautions:

- Connections should be tight
- Port and board selection should be correct
- Code should be written properly

Learning Outcomes:

Working of Circuit was verified uploading the program.